

Dissipation

SHOP NOW

ARROW
arrow.com

YAGEO

Joining the Global
Electronics Community

REGISTER | LOGIN

News | Video | Slideshows | Teardown | Education | EELife

About Us

Android | Automotive | Embedded | Industrial Control | Internet of Things | MCU | Medical | Memory | Open Source | PCB

NEWS & ANALYSIS: Apple Stops Royalties to Q'comm

designlines PROTOTYPING

Max's Cool Beans

MSGEQ7-Based DIY Audio Spectrum Analyzer: Construction

Max's Cool Beans

7/8/2014 07:30 PM EDT

41 comments post a comment

 3 saves
 LOGIN TO RATE

Like 18

Tweet

Share


G+

2

Here's a step-by-step guide to constructing a simple 14-band (2 x 7) audio spectrum analyzer using two MSGEQ7s and a chipKIT or Arduino microcontroller development platform.

Creating the first-pass hardware

When I started this project, I knew I was going to construct my first incarnation on a breadboard. One thing I needed was a 3.5mm stereo jack socket. I performed a web search and found a printed circuit board (PCB) mountable socket, so I ordered it. I'd foolishly assumed that something that said "PCB mountable" would have a traditional 0.1" pin pitch, and that its leads would be long enough to be used with a solderless breadboard. I was wrong on both counts. Eventually, I purchased a different [3.5mm PCB audio jack](#) and an associated [breakout board](#) from SparkFun.

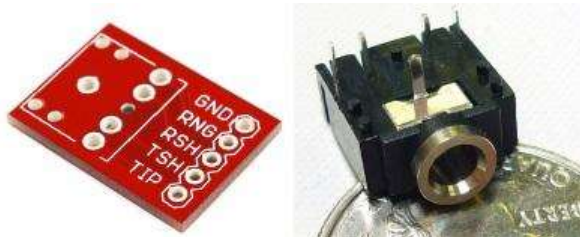

You'll also need some 0.1" pitch standard [male header pins](#), which -- as far as I recall -- don't come with the breakout board. Happily, I have loads of these lying around. Solder the jack on to the top of the breakout board, and solder a strip of five header pins on to the bottom of board (with the long ends pointing away from the board, so they can plug into the breadboard).

Let's move on to the breadboard itself. I'm using a full-sized solderless breadboard, similar to [this Adafruit board](#). I say "similar" because there are myriad tiny differences between such boards from different suppliers, but most of these are superficial.

Highly-Integrated RF Agile Transceivers

ANALOG
DEVICES
AHEAD OF WHAT'S POSSIBLE™ARROW
arrow.com

BUY NOW

Most Recent Comments




Don Swaab Joe experiences ground bounce caused by an improperly terminated cable.

 5/5/2017
 11:11:29 PM


Navigate to Related Links

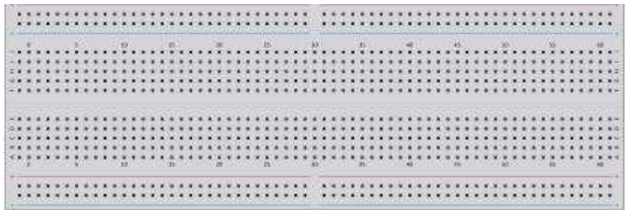[12 Views of a Science March](#)
[Skilled Labor, Free Trade Key Concerns over Brexit](#)
[Why Conflict Mineral Rules Improve the Supply Chain](#)
[Video Conferencing & Collaboration Leaps Forward](#)



(Click here for a larger image.)

Just in case you are new to all this, one important thing to note is that all the holes in the horizontal row under the red "+" line at the top of the board are connected together. Similarly, all the holes in the horizontal row above the blue "-" line at the top of the board are connected together. The same applies for the corresponding rows at the bottom of the board. In the fullness of time, we will connect our power supply to the "+" rows and our ground (GND) to the "-" rows.

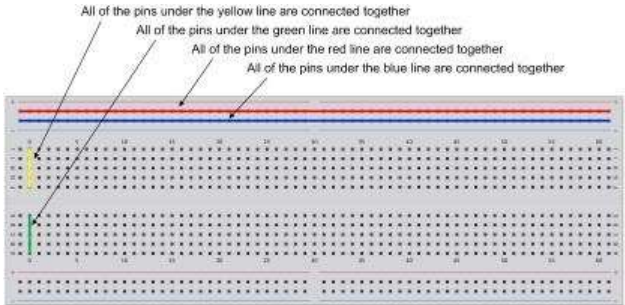


(Click here for a larger image.)

The really clever part is that the pins in each vertical column are connected together. If you look at the larger version of the above image, the A, B, C, D, and E pins in column 0 are connected together. Similarly, the F, G, H, I, and J pins in column 0 are connected together, and so forth for all the other columns.

As we previously noted, most of the differences between the boards from different manufactures are superficial -- the way they number the pins, for example. However, there can be the occasional gotcha. If you look at the large version of the first breadboard image above, you will see small gaps in the middle of the horizontal red (power) and blue (ground) lines. On some boards, this may indicate that the left and right sides are separate.

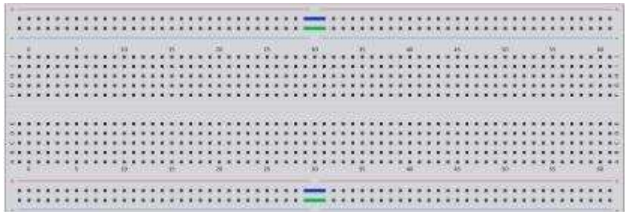This is exactly the way my board looks. I should have used my multimeter to check whether the two sides were separate. However, I was happily cruising along on autopilot, so I simply assumed that the two halves of the board were separated, and I proceeded to connect them together without thinking.



(Click here for a larger image.)

This leads us to the question of color coding one's wires. Given a choice, I usually use red and black wires to indicate power and ground connections, respectively. I subsequently use different colored wires to indicate various functions and types of signals. Thus, you might wonder about my using blue and green wires above. The answer is very pragmatic. When I started building this project, I quickly realized that I had only dries and drabs left in my various [pre-formed jumper wire kits](#), so I ended up using whatever was to hand at the time.

The next step is to add the audio jack/breakout board combo to the breadboard, and then add the two MSGEQ7s, as shown below.

Download Datasheets


PART NUMBER

e.g. LM317

Search

Cartoon Contest

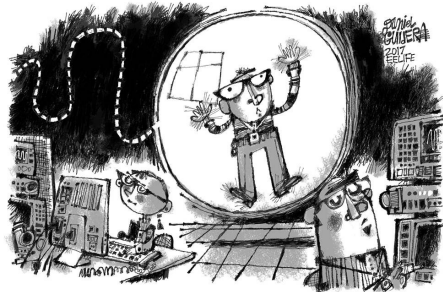May 2017 Cartoon Caption Contest: "Fun house"



"Your caption here!"

46 comments


ALL CARTOONS

Most Commented Most Popular

- 31 Shoot! What's the Dash Cam Say?
- 26 The Heart of a Soldering Station
- 25 Police Report Untangles Uber Crash Mystery
- 23 Intel Unveils 10, 22nm Processes
- 23 Solid State Batteries Aim to Top Li-ion
- 22 Where Do You Stand on Science March?
- 22 Intel Boots Drives with 3D XPoint
- 18 TSMC Expects First-Half Smartphone Slump
- 17 Engineering Ed Stuck in the Past
- 17 TSMC Tips 7+, 12, 22nm Nodes




Like Us on Facebook

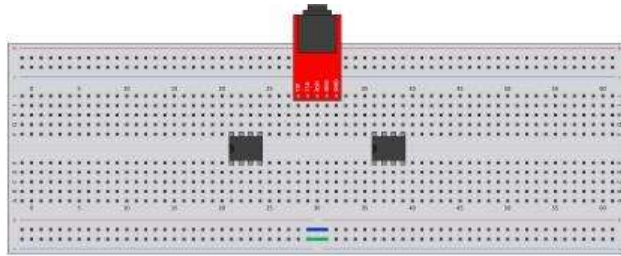


(Click [here](#) for a larger image.)

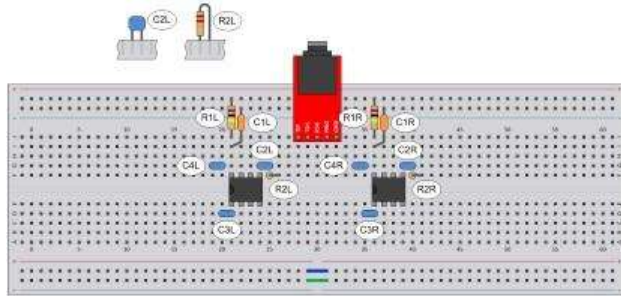Now we add the capacitors and resistors, as illustrated below. These component names match the schematic we showed earlier; the only difference is that we now have two channels, so each component name includes an 'L' or 'R' postfix indicating "Left" or "Right," respectively.




(Click [here](#) for a larger image.)

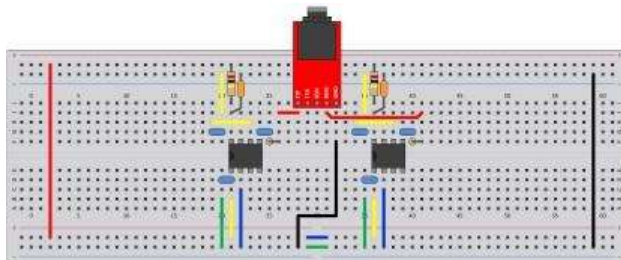Now it's time to add the wires. Observe the two red wires associated with the TIP and RNG ("Ring") pins on the audio-jack breakout board. These correspond to the left and right audio channels coming from the iPad. Don't worry about the TSH and RSH pins on the breakout board; we won't be using them.



(Click [here](#) for a larger image.)

Also observe the red wire on the left side of the board linking the two power rails and the black wire on the right side of the board linking the two ground rails. As you'll see in the photograph below, I started off by mounting these side by side, but I later moved the ground wire as shown in the graphic above purely for aesthetic reasons. Now, let's pause for a moment to take a sanity check and look at the real board.

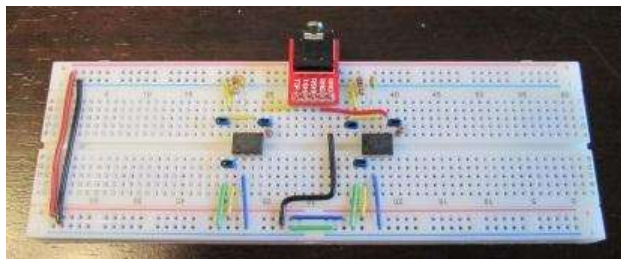

(Click [here](#) for a larger image.)

Did you spot the errors in the above photograph? (For the sake of charity, let's pretend these errors were "intentional" to make an educational point.) The thing is that, if you look closely at this photograph (and also at the next photograph shown below), you will observe that the wire from the TIP pin on the audio jack breakout board is directly connected to pin 5 of the left-hand

EE Times
17,997 likes

Like Page

Sign Up

Be the first of your friends to like this



EE Times on Twitter

follow us



EE Times Retweeted



Mike Demler @MikeDemler

.@Mobileye may currently hold a large lead in #ADAS processor market, but they're not the only game in town. @RenesasAmerica

11 Apr

EET

EE Times @eetimes

@MikeDemler thanks, Mike. The story is corrected!

09 Apr


EET

EE Times @eetimes

@MikeDemler Mentor's new platform could do away with each sensor module whose MCU is designed to do pre-processing to some degree.

MSGEQ7 chip. Similarly, the wire from the RNG pin on the breakout board is connected to pin 5 of the right-hand MSGEQ7 chip. In reality, the TIP and RNG pins should be connected to the "input sides" of resistors R2L and R2R, respectively (this is shown correctly in the graphical versions of these images). I discovered these mistakes as part of my test procedures (see also my [step-by-step test guide](#)).


The next step is to hook the breadboard up to the microcontroller board -- the chipKIT MAX32, in this example. For this, we use flexible [flying leads](#). We start by connecting one of the '+' power rails on the breadboard to the +3.3V power supply header pin on the chipKIT (or the +5V supply on an Arduino). We also connect one of the '-' ground rails on the breadboard to one of the two GND header pins on the chipKIT or Arduino. Personally, I don't think you can have a good enough ground connection, so I connected both GND header pins on the chipKIT, as shown below. I know there are additional power and ground connections on both chipKIT MAX32s and Arduino Megas. For the purposes of this guide, I'm just focusing on the ones on the main power header.

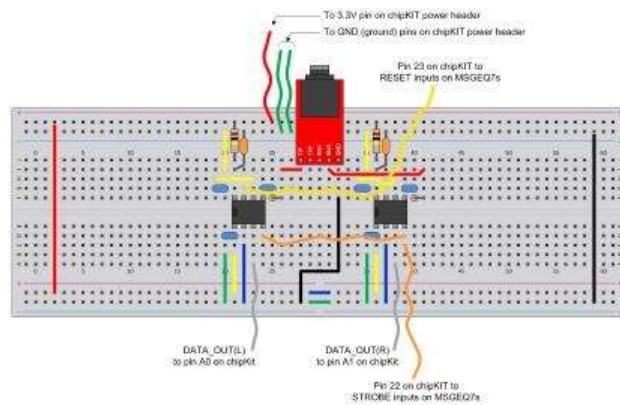

([Click here](#) for a larger image.)

The DATA_OUT from pin 3 on the left (and left channel) MSGEQ7 is connected to analog input A0 on the chipKIT. Similarly, the DATA_OUT from pin 3 on the right MSGEQ7 is connected to analog input A0 on the chipKIT.

Digital output pin 23 from the chipKIT is connected to the RESET input (pin 7) on the right MSGEQ7. A second flying lead is used to connect pin 7 on the right MSGEQ7 to pin 7 on the left MSGEQ7. Similarly, digital output pin 22 from the chipKIT is connected to the STROBE input (pin 4) on the right MSGEQ7. A second flying lead is used to connect pin 4 on the right MSGEQ7 to pin 4 on the left MSGEQ7. Once again, let's take a quick sanity check and look at a photograph of the current setup.

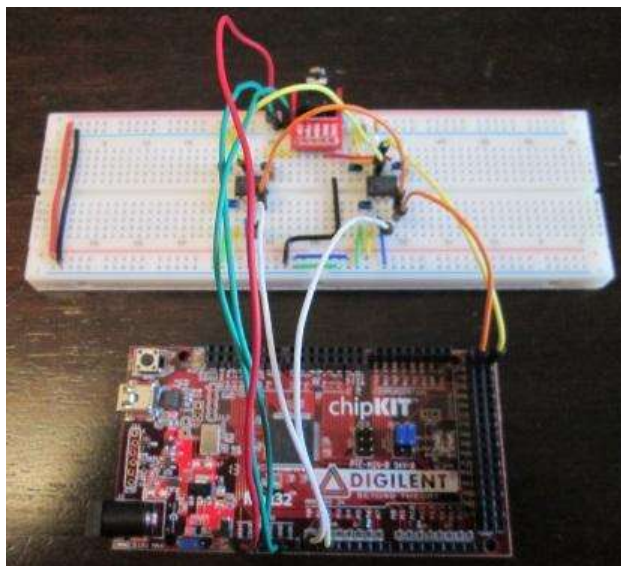

([Click here](#) for a larger image.)

IndexPage 1: [Introducing the MSGEQ7](#)Page 2: [Creating the first-pass hardware](#)Page 3: [Creating the first-pass software](#)Page 4: [Modifying the hardware to add the LEDs](#)Page 5: [Modifying the software to drive the LEDs](#)[To Page 3 >](#)[EMAIL THIS](#) [PRINT](#) [COMMENT](#)[< PREVIOUS PAGE 2 / 5 NEXT >](#)**Comments**VIEW COMMENTS: [NEWEST FIRST](#) | [OLDEST FIRST](#) | [THREADED VIEW](#)

PAGE 1 / 5 > >>

**Re: lacking vocals?**Clive "Max" Maxfield 9/9/2015
11:41:59 AMNO RATINGS
1 saves
[LOGIN TO RATE](#)USER RANK
AUTHOR@antedeluvian: *ROTFL- autocomplete, typo, modegreen or Freudian slip?*

My bad LOL

Even worse, when I first saw the Deja Vu album cover when I was a lad -- with all the arty-farty caligraphy, I read it as "Crosby Stills Nash & Donny" (instead of "Crosby Stills Nash & Young") ... so that's how I always think of them LOL

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)**Re: lacking vocals?**

antedeluvian 9/9/2015 11:28:03 AM

NO RATINGS
[LOGIN TO RATE](#)USER RANK
AUTHOR

Max

I've played "out house" by Crosby Stills & Nash

ROTFL- autocomplete, typo, modegreen or Freudian slip?

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)**Re: lacking vocals?**

sunneh 9/9/2015 10:00:25 AM

NO RATINGS
[LOGIN TO RATE](#)USER RANK
ROOKIE

Thanks for the quick response!

I havent scoped it yet, have bought a cheap version it should be on its way now.

do you think the timing could be the problem? i got everything set on 1000us (i figured hey it works) haha!!!

im using avr... so i think coding is a little different. my email is shangss@gmail.com thank you in advance :D

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)**Re: lacking vocals?**Max The Magnificent 9/9/2015
9:43:33 AMNO RATINGS
[LOGIN TO RATE](#)USER RANK
AUTHOR@sunneh: *I was wondering if you know of any problems with the msgeq7.*Hi there -- I haven't had any problems with my MSGEQ7s -- check out this blog (with embedded video) showing my BADASS Display <http://ubm.io/1FxDP2>.

I'm puzzled by your vocals problem -- I've played "out house" by Crosby Stills & Nash -- which is lagely vocals -- and it works great -- have you put a 'scope' on the input signal to see what's going in?

If you email me at max@clivemaxfield.com -- I'll send you the Arduino code I'm using to drive my BADASS display -- this includes the part that reads the data from the MSGEQ7s with the correct delays in it).

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)



lacking vocals?

sunneh 9/9/2015 7:52:23 AM

NO RATINGS
[LOGIN TO RATE](#)

USER RANK
ROOKIE

Hi there, saw your post, great vu meter :D

i was wondering if you know of any problems with the msgeq7.

So far mine is working great, but the led display does not move when there are vocals.

it only goes up and down when there is instrumentals. maybe it filtered out a frequency range? i am using lm386 to amplify the signal, otherwise the voltage would be too small

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)



Re: Input level for the MSGEQ7

Clive"Max"Maxfield 6/11/2015 1:31:29 PM

NO RATINGS
[LOGIN TO RATE](#)

USER RANK
AUTHOR

@jreza: I just watched your BADASS display and I have to say it discouraged me from building my own analyzer

It was that bad?

LOL

In the Coding Competition blog there's a link to the code I'm using for the BADASS Display. You could certainly create a much smaller version of the physical beast.

I agree that I feel really lucky being able to get components so easily.

I would love to see photos and video of your creation(s) -- maybe we could create a column around them...

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)



Re: Input level for the MSGEQ7

jreza 6/11/2015 1:18:52 PM

NO RATINGS
[LOGIN TO RATE](#)

USER RANK
ROOKIE

Max

Thanks for your quick response and all the info.

I just watched your BADASS display and I have to say it discouraged me from building my own analyzer :(, I know I'll never get close to that (just kidding! Baby steps). About the function generator and the shield, I live in Mexico, so it's kind of hard for me to try to get any of those (I barely got the MSGEQ7, I envy you and the way you get everything practically from around the corner :)

I'll take a deeper look at the posts when I get home.

When it is done I'll share some photos or video on what you've helped to build :)

Thanks a lot.

jreza

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)



Re: Input level for the MSGEQ7

Clive"Max"Maxfield 6/11/2015 11:38:21 AM

5 RATINGS
[LOGIN TO RATE](#)

USER RANK
AUTHOR

@Jezra: ...I have a question though...

You might also be interested in these related columns (I've included the link to this one because they form a set)

[Building a Low-Cost Frequency/Function Generator](#)

[Determining the Signal Characteristics of the iPad/iPod/iPhone Headphone Output](#)

[MSGEQ7-Based DIY Audio Spectrum Analyzer for BADASS Display](#)

[MSGEQ7-Based DIY Audio Spectrum Analyzer: Construction](#)

[MSGEQ7-Based DIY Audio Spectrum Analyzer: Testing](#)

[MSGEQ7-Based DIY Audio Spectrum Analyzer: Software & Timing](#)

BADASS Display Coding Competition

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)



USER RANK
AUTHOR

Re: Input level for the MSGEQ7
Clive "Max" Maxfield 6/11/2015
11:33:24 AM

NO RATINGS
[LOGIN TO RATE](#)

@Jreza: *What is the input level required by the MSGEQ7? Is it enough with just the output signal from a regular portable player? (from your tutorial it seems it does). Is it enough with the output level of a regular mic?*

Hi there -- I think you're going to really enjoy playing with this chip. Take a look at [This YouTube Video](#) showing two of these chips driving my BADASS Display.

I'm using the output from the headphone jack from my iPod (sometimes my iPad) with no problems at all -- typically I set the iPad to about 3/4 full volume to drive this chip -- then I control the actual sound volume using the amplifier driving the speakers.

I started off by creating a prototype using a breadboard (see [This YouTube Video](#)), but later my chum Duane Benson took my circuit and generated a special printed circuit board (PCB) for an Arduino Shield (this uses two MSGEQ7 chips -- one for each channel).



You can buy one of these boards from Duane from his [SteelPuppet.com](#) website if you wish.

Are you using an Arduino? If so, one of the things I do when I've just built a new sound analyzer card (I've now constructed three using Duane's shield for different projects) is to use the Serial I/O to display the numerical values on the screen so I can see what's happening -- you could use this technique to see how your microphone was working.

If you want to see some example Arduino code for this, email me at max@clivemaxfield.com and I'll send it to you.

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)



USER RANK
ROOKIE

Input level for the MSGEQ7
jreza 6/11/2015 10:14:43 AM

NO RATINGS
[LOGIN TO RATE](#)

Hi there.
I'm getting all the components to start this proyect. Thanks for the tutorial.
I have a question though, What is the input level required by the MSGEQ7? Is it enough with just the output signal from a regular portable player? (from your tutorial it seems it does). Is it enough with the output level of a regular mic?
Thanks
jreza

[Reply](#) [Post Message](#) [Messages List](#) [Start a Board](#)

ASPENCORE NETWORK

[EBN](#) | [EDN](#) | [EE Times](#) | [EEWeb](#) | [Electronic Products](#) | [Electronics-Tutorials](#) | [Embedded](#) | [Planet Analog](#) | [ElectroSchematics](#) | [Power Electronics News](#) | [TechOnline](#) | [Datasheets.com](#) | [Embedded Control Europe](#) | [Embedded Know How](#) | [Embedded News](#) | [IOT Design Zone](#) | [Motor Control Design](#) | [Electronics Know How](#) |

GLOBAL NETWORK

[EE Times Asia](#) | [EE Times China](#) | [EE Times India](#) | [EE Times Japan](#) | [EE Times Taiwan](#) | [EDN Asia](#) | [EDN China](#) | [EDN Taiwan](#) | [EDN Japan](#) | [ESM China](#) |

Working With Us: [About](#) | [Contact Us](#) | [Media Kits](#)

[Terms of Service](#) | [Privacy Statement](#) | [Copyright © 2017 AspenCore All Rights Reserved](#)